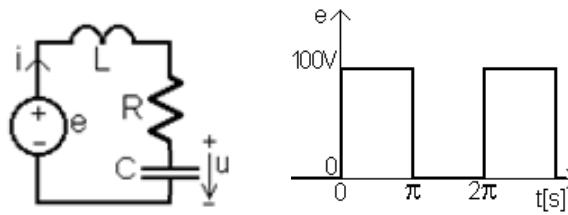


1) $R = 1 \Omega$, $L = 1 \text{ H}$, $C = 1 \text{ F}$. Find $u(t)$, $i(t)$



Step 1: Expand $e(t)$ into Fourier series

$$e(t) = E_o + \sum_{k=1}^{\infty} (C_k \cos(k\omega_o t) + S_k \sin(k\omega_o t))$$

$$\omega_o = \frac{2\pi}{T_o} = 1 \text{ rad/s}$$


$$E_o = \frac{1}{T_o} \int_0^{T_o} e(t) dt = \frac{1}{2\pi} \int_0^{\pi} 100 dt = 50 \text{ V}$$

$$C_k = \frac{2}{T_o} \int_0^{T_o} e(t) \cos(k\omega_o t) dt = \frac{1}{\pi} \int_0^{\pi} 100 \cos(kt) dt = 0$$

$$S_k = \frac{2}{T_o} \int_0^{T_o} e(t) \sin(k\omega_o t) dt = \frac{1}{\pi} \int_0^{\pi} 100 \sin(kt) dt = -\frac{100}{\pi k} \cos(kt) \Big|_0^{\pi} = -\frac{100}{\pi k} (\cos(k\pi) - 1)$$

$$= -\frac{100}{\pi k} ((-1)^k - 1) = \begin{cases} 0 & \text{for } k \text{ even} \\ \frac{200}{\pi k} & \text{for } k \text{ odd} \end{cases}$$
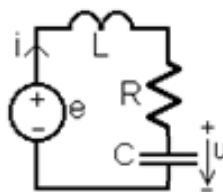
$$e(t) = 50 + \sum_{k=1}^{\infty} \frac{100}{k\pi} (1 - (-1)^k) \sin(kt) = 50 + \sum_{k=1,3,5,\dots}^{\infty} \frac{200}{k\pi} \sin(kt) [\text{V}]$$




Step 2: Find the DC component

$$E_o = 50 \text{ V}, \omega = 0 [\text{rad/s}]$$

$$\Rightarrow \frac{1}{j\omega C} = \infty [\Omega] \Rightarrow C \text{ is open circuit} \Rightarrow I_o = 0 [\text{A}]$$

$$j\omega L = 0 [\Omega] \Rightarrow L \text{ is short circuit}$$
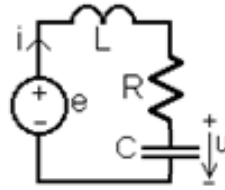
$$\text{KVL} \Rightarrow U_o = 50 [\text{V}]$$



$$e(t) = 50 + \sum_{k=1,3,5,\dots}^{\infty} \frac{200}{k\pi} \sin(kt) [\text{V}]$$

Step 3: Find the k^{th} harmonic

$$e_k(t) = \frac{200}{k\pi} \sin(kt) [\text{V}], \quad k \text{ odd}$$

$$\omega = k [\text{rad/s}] \Rightarrow Z = R + j\omega L + \frac{1}{j\omega C} = 1 + j(k - \frac{1}{k}) [\Omega]$$

$$Z = \sqrt{1 + \left(k - \frac{1}{k}\right)^2} \angle \arctg(k - \frac{1}{k}) [\Omega]$$

$$\Rightarrow i_k(t) = \frac{200}{k\pi \sqrt{1 + \left(k - \frac{1}{k}\right)^2}} \sin(kt - \arctg(k - \frac{1}{k})) [\text{A}]$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{jk} = \frac{1}{k} \angle -90^\circ [\Omega]$$


$$\Rightarrow u_k(t) = \frac{200}{k^2 \pi \sqrt{1 + \left(k - \frac{1}{k}\right)^2}} \sin(kt - \arctg(k - \frac{1}{k}) - 90^\circ) [\text{V}]$$

Step 4: Apply the superposition principle


$$i(t) = \sum_{k=1,3,5,\dots}^{\infty} \frac{200}{k\pi \sqrt{1 + \left(k - \frac{1}{k}\right)^2}} \sin(kt - \arctg(k - \frac{1}{k})) [\text{A}]$$

$$u(t) = 50 + \sum_{k=1,3,5}^{+\infty} \frac{200}{k^2 \pi \sqrt{1 + \left(k - \frac{1}{k}\right)^2}} \sin(kt - \arctg(k - \frac{1}{k}) - 90^\circ) [\text{V}]$$

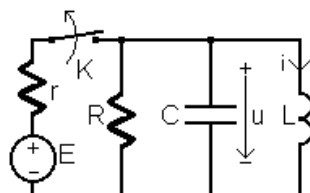- 2) $E = 100 \text{ V (DC)}$, $r = R = 100 \Omega$, $L = 100 \text{ mH}$, $C = 10 \mu\text{F}$. $t < 0$: K closed. $t > 0$: K open. Find $u(t), i(t)$




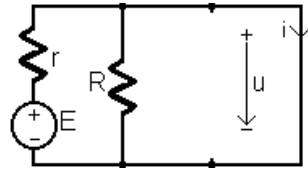$t < 0$: K is closed for very long time \Rightarrow the circuit is in DC steady-state (since E is a DC voltage source) \Rightarrow C acts as an open circuit and L acts as a short circuit $\Rightarrow u = 0$ V, $i = E/r = 1$ A.



$t > 0$: K is open.
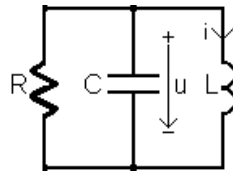
$$\text{KCL} \Rightarrow \frac{u}{R} + C \frac{du}{dt} + i = 0$$



Natural response: Taking derivative and applying the fact that $u = L \frac{di}{dt}$, one gets

$$\frac{L}{R} \frac{di}{dt} + CL \frac{d^2 i}{dt^2} + i = 0$$

$$\frac{L}{R} p + CL p^2 + 1 = 0$$

$$\frac{1}{RC} p + p^2 + \frac{1}{LC} = 0$$

$$\Rightarrow \frac{1}{R} \frac{du}{dt} + C \frac{d^2 u}{dt^2} + \frac{u}{L} = 0 \Rightarrow \frac{d^2 u}{dt^2} + \frac{1}{RC} \frac{du}{dt} + \frac{1}{LC} u = 0$$

The characteristic equation: $p^2 + \frac{1}{RC} p + \frac{1}{LC} = 0$

$$\Rightarrow p = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -500 \pm j 500\sqrt{3}$$

$$\Rightarrow i_n(t) = A_1 e^{-500t} \cos(500\sqrt{3} t + A_2) \text{ [A]}$$

Forced response: $i_f(t) = 0$ [A]

Complete response: $i(t) = i_f(t) + i_n(t) = A_1 e^{-500t} \cos(500\sqrt{3} t + A_2)$ [A]

$$u(t) = L \frac{di}{dt} = -50 A_1 e^{-500t} \cos(500\sqrt{3} t + A_2) - 50\sqrt{3} A_1 e^{-500t} \sin(500\sqrt{3} t + A_2) \text{ [V]}$$

$$i(0^+) = i(0^-) = 1 \text{ (current through inductor is continuous)} \Rightarrow A_1 \cos(A_2) = 1$$

$$u(0^+) = u(0^-) = 0 \text{ (voltage across capacitor is continuous)}$$


$$\Rightarrow A_1 \cos(A_2) + \sqrt{3} A_1 \sin(A_2) = 0 \Rightarrow \sqrt{3} A_1 \sin(A_2) = -1 \Rightarrow A_1 \sin(A_2) = -\frac{1}{\sqrt{3}}$$

$$\Rightarrow \tan(A_2) = -\frac{1}{\sqrt{3}} \Rightarrow A_2 = -30^\circ \Rightarrow A_1 = \frac{2}{\sqrt{3}}$$


$$i(t) = \frac{2}{\sqrt{3}} e^{-500t} \cos(500\sqrt{3}t - 30^\circ) \text{ [A]}$$

$$u(t) = -\frac{100}{\sqrt{3}} e^{-500t} \cos(500\sqrt{3}t - 30^\circ) - 100e^{-500t} \sin(500\sqrt{3}t - 30^\circ) \text{ [V]}$$

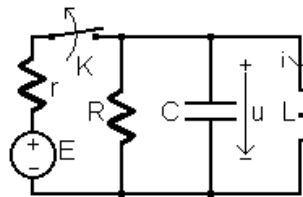
- 2) $E = 100 \text{ V(DC)}$, $r = R = 100 \Omega$, $L = 100 \text{ mH}$, $C = 10 \mu\text{F}$. $t < 0$: K closed. $t > 0$: K open. Find $u(t), i(t)$



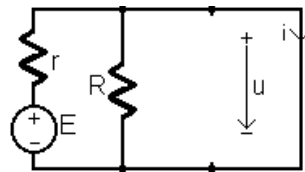$t < 0$: K is closed for very long time \Rightarrow the circuit is in DC steady-state (since E is a DC voltage source) \Rightarrow C acts as an open circuit and L acts as a short circuit $\Rightarrow u = 0 \text{ V}$, $i = E/r = 1 \text{ A}$.



$t > 0$: K is open.

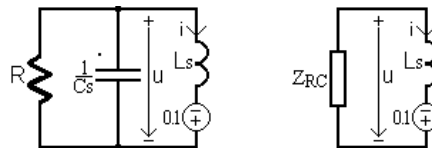

$$Z_{RC} = \frac{R \frac{1}{C_s}}{R + \frac{1}{C_s}} = \frac{R}{RCs + 1} = \frac{10^5}{s + 1000}$$

$$\text{KVL: } -0.1 + (Z_{RC} + Ls)I(s) = 0$$

$$\Rightarrow I(s) = \frac{0.1}{\frac{10^5}{s+1000} + 0.1s} = \frac{0.1(s+1000)}{0.1s^2 + 100s + 10^5} = \frac{s+1000}{s^2 + 10^3s + 10^6} = \frac{s+500+500}{(s+500)^2 + (500\sqrt{3})^2}$$

$$\Rightarrow i(t) = e^{-500t} \cos(500\sqrt{3}t) + \frac{1}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3}t) \text{ [A]}$$

$$i(t) = \frac{2}{\sqrt{3}} e^{-500t} \cos(500\sqrt{3}t - 30^\circ) \text{ [A]}$$

$$= \frac{2}{\sqrt{3}} e^{-500t} [\cos(30^\circ)\cos(500\sqrt{3}t) + \sin(30^\circ)\sin(500\sqrt{3}t)]$$

$$= \frac{2}{\sqrt{3}} e^{-500t} \left[\frac{\sqrt{3}}{2} \cos(500\sqrt{3}t) + \frac{1}{2} \sin(500\sqrt{3}t) \right]$$

$$= e^{-500t} [\cos(500\sqrt{3}t) + \frac{1}{\sqrt{3}} \sin(500\sqrt{3}t)]$$

$$\text{KVL} \Rightarrow LsI(s) - 0.1 - U(s) = 0$$

$$\Rightarrow U(s) = LsI(s) - 0.1 = \frac{0.1s(s+1000)}{s^2 + 10^3s + 10^6} - 0.1 = \frac{0.1s(s+1000) - 0.1(s^2 + 10^3s + 10^6)}{s^2 + 10^3s + 10^6}$$

$$= \frac{-10^5}{s^2 + 10^3s + 10^6} = \frac{-10^5}{(s+500)^2 + (500\sqrt{3})^2}$$

$$\Rightarrow u(t) = -\frac{200}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3}t) \text{ [V]}$$

3) Given the circuit in Fig.1 with $R = 10 \text{ k}\Omega$, $C = 1 \text{ }\mu\text{F}$.

a) Find the voltage transfer function $K_u(j\omega) = \frac{\dot{U}_2}{\dot{U}_1}$

b) Find $u_2(t)$ if $u_1(t) = 100 + 100\sin(500t) + 100\sin(1000t) \text{ mV}$

Solution

a) Find the voltage transfer function $K_u(j\omega) = \frac{\dot{U}_2}{\dot{U}_1}$

$$Z_1 = \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega CR}$$



$$Z_2 = R + \frac{1}{j\omega C} = \frac{1 + j\omega CR}{j\omega C}$$

$$\dot{U}_- = \frac{Z_2}{Z_1 + Z_2} \dot{U}_2 = \dot{U}_+ = \dot{U}_1$$

$$\Rightarrow K_u(j\omega) = \frac{\dot{U}_2}{\dot{U}_1} = \frac{Z_1 + Z_2}{Z_2} = 1 + \frac{Z_1}{Z_2} = 1 + \frac{j\omega CR}{(1 + j\omega CR)^2}$$

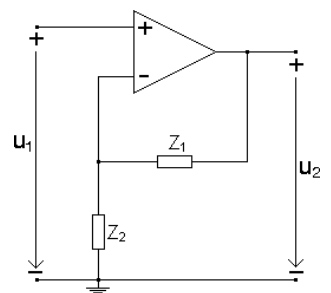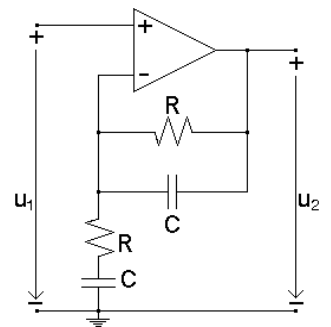b) Find $u_2(t)$ if $u_1(t) = 100 + 100\sin(500t) + 100\sin(1000t) \text{ mV}$.

DC component: $u_{10} = 100 \text{ mV}$, $\omega = 0 \text{ rad/s}$



$$K_U(0) = \frac{\dot{U}_{20}}{\dot{U}_{10}} = 1 \Rightarrow u_{20} = 100 \text{ V}$$

AC component with $\omega = 500 \text{ rad/s}$: $u_{11} = 100\sin(500t) \text{ mV}$

$$\begin{aligned} K_U(j500) &= \frac{\dot{U}_{21}}{\dot{U}_{11}} = 1 + \frac{j500 \cdot 10^{-6} \cdot 10^4}{(1 + j500 \cdot 10^{-6} \cdot 10^4)^2} = 1 + \frac{j5}{(1 + j5)^2} = \frac{1 - 5 + j10 + j5}{(1 + j5)^2} \\ &= \frac{-4 + j15}{(1 + j5)^2} = \frac{-4 + j15}{(1 + j5)^2} = \frac{15.5 \angle 105^\circ}{26 \angle 157.4^\circ} = 0.6 \angle -52.4^\circ \end{aligned}$$

$$\Rightarrow u_{21}(t) = 60\sin(500t - 52.4^\circ) \text{ mV}$$

AC component with $\omega = 1000 \text{ rad/s}$: $u_{12} = 100\sin(1000t) \text{ mV}$

$$\begin{aligned} K_U(j1000) &= \frac{\dot{U}_{22}}{\dot{U}_{12}} = 1 + \frac{j10}{(1 + j10)^2} = \frac{1 - 100 + j20 + j10}{(1 + j10)^2} = \frac{-99 + j30}{(1 + j10)^2} \\ &= \frac{103.4 \angle 163^\circ}{10 \angle 168.6^\circ} = 10.34 \angle -5.6^\circ \end{aligned}$$

$$\Rightarrow u_{22}(t) = 1034\sin(1000t - 5.6^\circ) \text{ mV}$$

Superposition:

$$\Rightarrow u_o(t) = 100 + 60\sin(500t - 52.4^\circ) + 1034\sin(1000t - 5.6^\circ) \text{ mV}$$

4) The circuit in Fig.2A has $R = 1 \Omega$, $C = 1 \text{ F}$. e is a periodic voltage source with period $T_o = 2\pi \text{ s}$ (Fig.2B). Expand $e(t)$ into Fourier series. Find an expression of $u(t)$

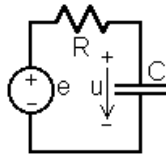


Fig.2A

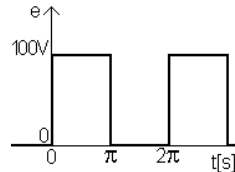


Fig.2B

Step 1: Expand $e(t)$ into Fourier series

$$e(t) = E_o + \sum_{k=1}^{\infty} (C_k \cos(k\omega_o t) + S_k \sin(k\omega_o t))$$

$$\omega_o = \frac{2\pi}{T_o} = 1 \text{ rad/s}$$

$$E_o = \frac{1}{T_o} \int_0^{T_o} e(t) dt = \frac{1}{2\pi} \int_0^{\pi} 100 dt = 50 \text{ V}$$

$$C_k = \frac{2}{T_o} \int_0^{T_o} e(t) \cos(k\omega_o t) dt = \frac{1}{\pi} \int_0^{\pi} 100 \cos(kt) dt = 0$$


$$S_k = \frac{2}{T_o} \int_0^{T_o} e(t) \sin(k\omega_o t) dt = \frac{1}{\pi} \int_0^\pi 100 \sin(kt) dt = -\frac{100}{\pi k} \cos(kt) \Big|_0^\pi = -\frac{100}{\pi k} (\cos(k\pi) - 1)$$

$$= -\frac{100}{\pi k} ((-1)^k - 1) = \begin{cases} 0 & \text{for } k \text{ even} \\ \frac{200}{\pi k} & \text{for } k \text{ odd} \end{cases}$$

$$e(t) = 50 + \sum_{k=1}^{\infty} \frac{100}{k\pi} (1 - (-1)^k) \sin(kt) = 50 + \sum_{k=1,3,5,\dots}^{\infty} \frac{200}{k\pi} \sin(kt) \text{ [V]}$$

Step 2: Find the DC component
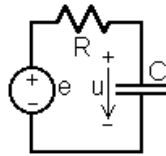
$$\omega = 0 \text{ [rad/s]} \Rightarrow \frac{1}{j\omega C} = \infty \text{ [\Omega]} \Rightarrow C \text{ is open circuit} \Rightarrow U_o = 50 \text{ [V]}$$



Step 3: Find the k^{th} harmonic

$$e_k(t) = \frac{200}{k\pi} \sin(kt) \quad k \text{ odd}$$

$$\omega = k \text{ [rad/s]} \Rightarrow Z = R + \frac{1}{j\omega C} = 1 + \frac{1}{jk} = 1 - j\frac{1}{k} = \sqrt{1 + \frac{1}{k^2}} \angle -\arctg\left(\frac{1}{k}\right) \text{ [\Omega]}$$

$$\Rightarrow i_k(t) = \frac{200}{k\pi \sqrt{1 + \frac{1}{k^2}}} \sin\left(kt + \arctg\left(\frac{1}{k}\right)\right) \text{ [A]}$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{jk} = \frac{1}{k} \angle -90^\circ$$

$$\Rightarrow u_k(t) = \frac{200}{k^2 \pi \sqrt{1 + \frac{1}{k^2}}} \sin\left(kt + \arctg\left(\frac{1}{k}\right) - 90^\circ\right) \text{ [V]}$$

Step 4: Apply the superposition principle

$$u(t) = 50 + \sum_{k=1,3,5}^{+\infty} \frac{200}{k^2 \pi \sqrt{1 + \frac{1}{k^2}}} \sin\left(kt + \arctg\left(\frac{1}{k}\right) - 90^\circ\right) \text{ [V]}$$

$$i(t) = \sum_{k=1,3,5}^{+\infty} \frac{200}{k\pi \sqrt{1 + \frac{1}{k^2}}} \sin\left(kt + \arctg\left(\frac{1}{k}\right)\right) \text{ [V]}$$

5. Consider the circuit in Fig.3 with $E = 100 \text{ V}$, $r = 10 \Omega$, $R = 100 \Omega$, $L = 0.1 \text{ H}$. Initially the switch K is closed for very long time and suddenly open at $t = 0$. Find $u(t)$ and $i(t)$.

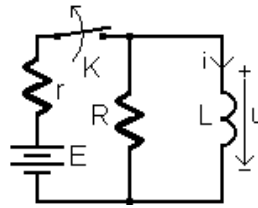


Fig.3

$t < 0$:


K is closed for very long time \Rightarrow the circuit is operating in DC steady-state
 \Rightarrow the inductor acts as a short circuit $\Rightarrow u = 0 \text{ V}$

$$i_2 = u/R = 0/100 = 0 \text{ A}$$


$$\text{KCL: } i_1 - i_2 - i = 0 \Rightarrow i_1 = i$$

$$\text{KVL: } -E + ri_1 + u = 0 \Rightarrow i_1 = E/r$$

$$\Rightarrow i = E/r = 10 \text{ A}$$

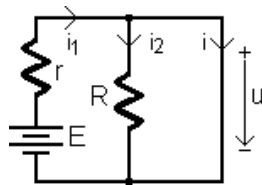

$t > 0$: K is open

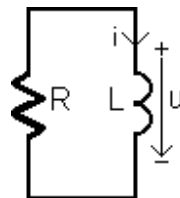

$$\text{KVL: } L \frac{di}{dt} + Ri = 0$$

Natural response:

The characteristic equation: $pL + R = 0$

$$\Rightarrow p = -\frac{R}{L} = -1000 \Rightarrow i_n(t) = Ce^{-1000t} \text{ [A]}$$


Forced response: $i_f(t) = 0 \text{ [A]}$

Complete response: $i(t) = i_f(t) + i_n(t) = Ce^{-1000t} \text{ [A]}$

Initial conditions: $i(0^+) = i(0^-) = 10 = C$ (current through inductor is continuous)

$$\Rightarrow i(t) = 10e^{-1000t} \text{ [A]}$$
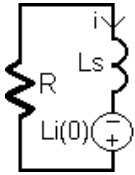
$$\Rightarrow u(t) = L \frac{di}{dt} = -1000e^{-1000t} \text{ [V]}$$



$$\text{KVL: } RI(s) + LsI(s) - Li(0) = 0$$

$$I(s) = Li(0)/(Ls + R) = 1/(0.1s + 100) = 10/(s + 1000)$$

$$\Rightarrow i(t) = 10e^{-1000t} \text{ A}$$

$$U(s) = LsI(s) - Li(0) = s/(s + 1000) - 1 = 1000/(s + 1000)$$

$$\Rightarrow u(t) = 1000e^{-1000t} \text{ V}$$

6. The circuit in Fig.4 has $E = 100\text{V}$ (DC), $R = 100 \Omega$, $L = 100 \text{ mH}$, $C = 10 \mu\text{F}$. The switch K is open for very long time and is closed at $t = 0$. Find $u(t)$.



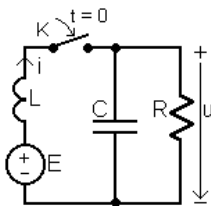


Fig.4

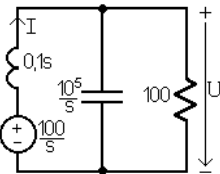

$$Z_{RC} = \frac{\frac{10^5}{s} \cdot 100}{\frac{10^5}{s} + 100}$$

$$= \frac{10^5}{s + 10^3}$$

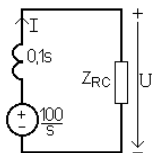

KVL:

$$- \frac{100}{s} + (0.1s + Z_{RC})I(s) = 0$$

$$U(s) = Z_{RC}I(s)$$

$t < 0$: K is open for very long time $\Rightarrow i = 0 \text{ [A]}$, $u = 0 \text{ [V]}$

$t > 0$: K is closed

$$U \left(\frac{10}{s} + \frac{s}{10^5} + \frac{1}{100} \right) = \frac{10^3}{s^2}$$

$$U \left(\frac{10^6 + s^2 + 10^3 s}{10^5 s} \right) = \frac{10^3}{s^2}$$

$$\Rightarrow U = \frac{10^8}{s(s^2 + 10^3 s + 10^6)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 10^3 s + 10^6}$$

$$= \frac{(A + B)s^2 + (10^3 A + C)s + 10^6 A}{s(s^2 + 10^3 s + 10^6)}$$

$$\Rightarrow A + B = 0$$


$$10^3 A + C = 0$$

$$10^6 A = 10^8$$


$$U(s) = \frac{100}{s} - \frac{100s + 10^5}{s^2 + 10^3 s + 10^6}$$

$$= \frac{100}{s} - \frac{100(s + 500)}{(s + 500)^2 + (500\sqrt{3})^2} - \frac{5 \times 10^4}{(s + 500)^2 + (500\sqrt{3})^2}$$
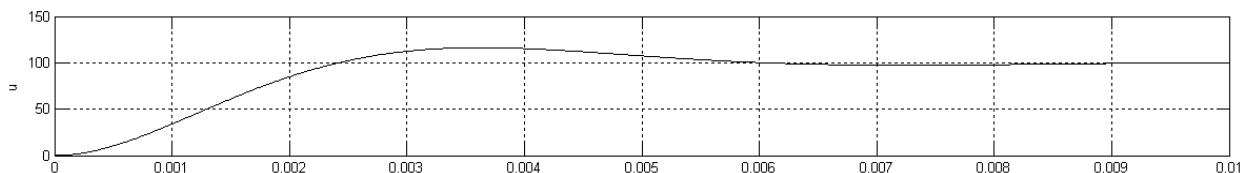
$$\Rightarrow u(t) = 100 - 100e^{-500t} \cos(500\sqrt{3} t) - \frac{100}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3} t) \text{ [V]}$$






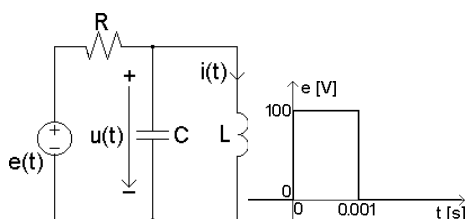7. Given the circuit in Fig.E4.5 with $R = 100 \, \Omega$, $L = 100 \, \text{mH}$, $C = 10 \, \mu\text{F}$. Find $u(t)$ and $i(t)$.




$t < 0$: $e = 0 \, \text{V} \Rightarrow u(t) = 0 \, \text{V}$ and $i(t) = 0 \, \text{A}$

$t > 0$:

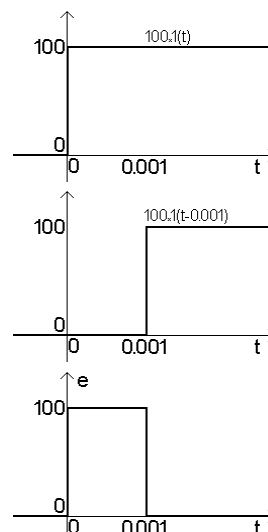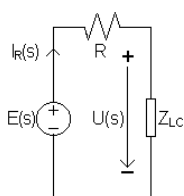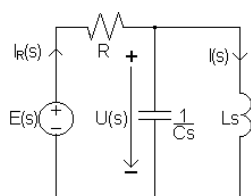

$$1^{\text{st}} \text{ method: } e(t) = 100.1(t) - 100.1(t-0.001) \Rightarrow E(s) = \frac{100}{s} - \frac{100}{s} e^{-0.001s} = \frac{100}{s} (1 - e^{-0.001s})$$

$$2^{\text{nd}} \text{ method: } E(s) = \int_0^{+\infty} e(t) e^{-st} dt = \int_0^{0.001} 100 e^{-st} dt = \frac{100 e^{-st}}{-s} \Big|_0^{0.001} = \frac{100(1 - e^{-0.001s})}{s}$$
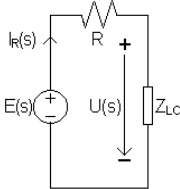
$$Z_{LC} = \frac{Ls \frac{1}{Cs}}{Ls + \frac{1}{Cs}} = \frac{Ls}{LCs^2 + 1}$$


$$\text{KVL: } -E(s) + (R + Z_{LC})I_R(s) = 0 \Rightarrow I_R(s) = \frac{E(s)}{R + Z_{LC}}$$

$$U(s) = Z_{LC} I_R(s) = \frac{Z_{LC} E(s)}{R + Z_{LC}} = \frac{\frac{Ls}{LCs^2 + 1} E(s)}{R + \frac{Ls}{LCs^2 + 1}} = \frac{\frac{0.1s}{10^{-6}s^2 + 1} E(s)}{100 + \frac{0.1s}{10^{-6}s^2 + 1}} = \frac{\frac{10^5 s}{s^2 + 10^6} E(s)}{100 + \frac{10^5 s}{s^2 + 10^6}}$$

$$= \frac{10^3 s E(s)}{s^2 + 10^3 s + 10^6} = \frac{10^5}{s^2 + 10^3 s + 10^6} (1 - e^{-0.001s}) = \frac{10^5}{(s+500)^2 + (500\sqrt{3})^2} (1 - e^{-0.001s})$$

$$\frac{10^5}{(s+500)^2 + (500\sqrt{3})^2} \leftrightarrow \frac{200}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3} t)$$

$$\frac{10^5}{(s+500)^2 + (500\sqrt{3})^2} e^{-0.001s} \leftrightarrow \frac{200}{\sqrt{3}} e^{-500(t-0.001)} \sin(500\sqrt{3} (t-0.001)) 1(t-0.001)$$

$$\Rightarrow u(t) = \frac{200}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3} t) - \frac{200}{\sqrt{3}} e^{-500(t-0.001)} \sin(500\sqrt{3} (t-0.001)) 1(t-0.001) \text{ V}$$

$$I(s) = \frac{U(s)}{Ls} = \frac{10^6}{s(s^2 + 10^3 s + 10^6)} (1 - e^{-0.001s}) = \left(\frac{1}{s} - \frac{10^3}{s^2 + 10^3 s + 10^6} \right) (1 - e^{-0.001s})$$


$$= \left(\frac{1}{s} - \frac{10^3}{(s+500)^2 + (500\sqrt{3})^2} \right) (1 - e^{-0.001s})$$

$$\frac{1}{s} - \frac{10^3}{(s+500)^2 + (500\sqrt{3})^2} \leftrightarrow 1 - \frac{2}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3} t)$$

$$\left(\frac{1}{s} - \frac{10^3}{(s+500)^2 + (500\sqrt{3})^2} \right) e^{-0.001s} \leftrightarrow \left(1 - \frac{2}{\sqrt{3}} e^{-500(t-0.001)} \sin(500\sqrt{3} (t-0.001)) \right) 1(t-0.001)$$

$$\Rightarrow i(t) = 1 - \frac{2}{\sqrt{3}} e^{-500t} \sin(500\sqrt{3} t) - \left(1 - \frac{2}{\sqrt{3}} e^{-500(t-0.001)} \sin(500\sqrt{3} (t-0.001)) \right) 1(t-0.001) \text{ A}$$

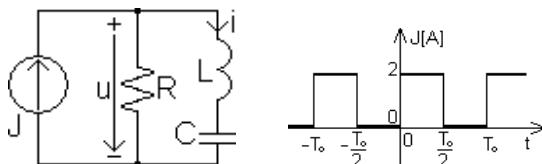8. The circuit in Fig.E3.4 has $R = 1\Omega$, $L = 1\text{H}$, $C = 1\text{F}$. J is a periodic current source with period $T_0 = 2\pi$ [s]. Expand $J(t)$ into Fourier series. Find an expression of $u(t)$ and $i(t)$.



Step 1: Expand $J(t)$ into Fourier series

$$J(t) = J_0 + \sum_{k=1}^{\infty} (C_k \cos(k\omega_0 t) + S_k \sin(k\omega_0 t))$$

$$\omega_o = \frac{2\pi}{T_o} = 1 \text{ [rad/s]}$$

$$J_o = \frac{1}{T_o} \int_0^{T_o} J(t) dt = \frac{1}{2\pi} \int_0^\pi 2 dt = 1 \text{ [A]}$$


$$C_k = \frac{2}{T_o} \int_0^{T_o} J(t) \cos(k\omega_o t) dt = \frac{1}{\pi} \int_0^\pi 2 \cos(kt) dt = 0$$

$$S_k = \frac{2}{T_o} \int_0^{T_o} J(t) \sin(k\omega_o t) dt = \frac{1}{\pi} \int_0^\pi 2 \sin(kt) dt = -\frac{2}{\pi k} \cos(kt) \Big|_0^\pi = -\frac{2}{\pi k} (\cos(k\pi) - 1)$$

$$= \frac{2}{\pi k} (1 - (-1)^k) = \begin{cases} 0 & \text{for } k \text{ even} \\ \frac{4}{\pi k} & \text{for } k \text{ odd} \end{cases}$$

$$J(t) = 1 + \sum_{k=1}^{\infty} \frac{2}{k\pi} (1 - (-1)^k) \sin(kt) = 1 + \sum_{k=1,3,5,\dots}^{\infty} \frac{4}{k\pi} \sin(kt) \text{ [A]}$$


Step 2: Find the DC component

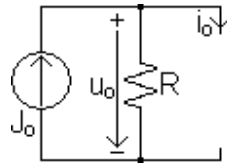

$$\omega = 0 \text{ [rad/s]} \Rightarrow \frac{1}{j\omega C} = \infty \text{ [\Omega]} \Rightarrow C \text{ is open circuit} \Rightarrow I_o = 0 \text{ [A]}, U_o = RJ_o = 1 \text{ [V]}$$

$$j\omega L = 0 \Rightarrow L \text{ is short circuit}$$

Step 3: Find the k^{th} harmonic

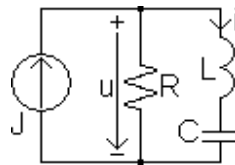

$$J_k(t) = \frac{4}{k\pi} \sin(kt) \leftrightarrow \dot{J}_k = \frac{4}{k\pi} \angle 0 \quad k \text{ odd}$$


$$\omega = k \text{ [rad/s]}$$

$$Z = \frac{R(j\omega L + \frac{1}{j\omega C})}{R + j\omega L + \frac{1}{j\omega C}} = \frac{jk + \frac{1}{jk}}{1 + jk + \frac{1}{jk}} = \frac{1 - k^2}{1 - k^2 + jk} = \frac{k^2 - 1}{k^2 - 1 - jk}$$

$$= \frac{k^2 - 1}{\sqrt{(k^2 - 1)^2 + k^2}} \angle \arctg\left(\frac{k}{k^2 - 1}\right)$$

$$\Rightarrow \dot{U}_k = Z \dot{J}_k = \frac{k^2 - 1}{\sqrt{(k^2 - 1)^2 + k^2}} \angle \arctg\left(\frac{k}{k^2 - 1}\right) \cdot \frac{4}{k\pi} \angle 0 = \frac{4(k^2 - 1)}{k\pi\sqrt{(k^2 - 1)^2 + k^2}} \angle \arctg\left(\frac{k}{k^2 - 1}\right)$$
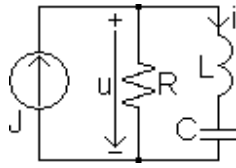
$$\Rightarrow u_k(t) = \frac{4(k^2 - 1)}{k\pi\sqrt{(k^2 - 1)^2 + k^2}} \sin(kt + \arctg\left(\frac{k}{k^2 - 1}\right)) \text{ [V]}$$



$$\begin{aligned} \dot{I}_k &= \frac{\dot{U}_k}{j\omega L + \frac{1}{j\omega C}} = \frac{\dot{U}_k}{jk + \frac{1}{jk}} = \frac{jk\dot{U}_k}{1 - k^2} = \frac{k}{1 - k^2} \angle 90^\circ \cdot \frac{4(k^2 - 1)}{k\pi\sqrt{(k^2 - 1)^2 + k^2}} \angle \arctg\left(\frac{k}{k^2 - 1}\right) \\ &= \frac{-4}{\pi\sqrt{(k^2 - 1)^2 + k^2}} \angle 90^\circ + \arctg\left(\frac{k}{k^2 - 1}\right) \text{ [A]} \end{aligned}$$

$$\Rightarrow i_k(t) = \frac{-4}{\pi\sqrt{(k^2 - 1)^2 + k^2}} \sin(kt + 90^\circ + \arctg\left(\frac{k}{k^2 - 1}\right)) \text{ [A]}$$

Step 4: Apply the superposition principle

$$u(t) = 1 + \sum_{k=1,3,5,\dots}^{\infty} \frac{4(k^2 - 1)}{k\pi\sqrt{(k^2 - 1)^2 + k^2}} \sin(kt + \arctg\left(\frac{k}{k^2 - 1}\right)) \text{ [V]}$$

$$i(t) = \sum_{k=1,3,5,\dots}^{\infty} \frac{-4}{\pi\sqrt{(k^2 - 1)^2 + k^2}} \sin(kt + \arctg\left(\frac{1}{k^2 - 1}\right) + 90^\circ) \text{ [A]}$$

3.10 Find the Thevenin equivalent circuit of the two-terminal networks in Fig.E3.10. Deduce the maximum power delivered by the two-terminal network.

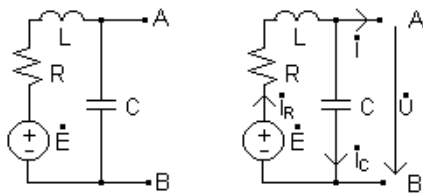


Fig.E3.10

$$\dot{I}_C = \frac{\dot{U}}{1} = j\omega C \dot{U}$$

$$\text{KCL: } \dot{I}_R = \dot{I}_C + \dot{I} = j\omega C \dot{U} + \dot{I}$$

$$\text{KVL: } -\dot{E} + (R + j\omega L) \dot{I}_R + \dot{U} = 0$$

$$\Rightarrow -\dot{E} + (R + j\omega L)(j\omega C \dot{U} + \dot{I}) + \dot{U} = 0$$


$$(R + j\omega L) \dot{I} + (R + j\omega L)j\omega C \dot{U} + \dot{U} = \dot{E}$$

$$\dot{E}_T = \dot{U}|_{i=0} = \frac{\dot{E}}{1 + j\omega C(R + j\omega L)}$$

$$\dot{J}_N = \dot{I}|_{\dot{U}=0} = \frac{\dot{E}}{R + j\omega L}$$

$$Z_T = \dot{E}_T / \dot{J}_N = \frac{R + j\omega L}{1 + j\omega C(R + j\omega L)}$$

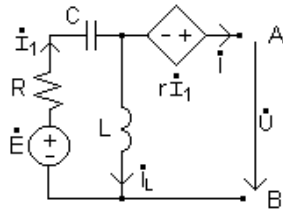Find the Thevenin equivalent circuit of the two-terminal networks in Fig.E3.10. Deduce the maximum power delivered by the two-terminal network.



$$\text{KCL: } \dot{I}_1 = \dot{I}_L + \dot{I}$$

$$\text{KVL: } -j\omega L \dot{I}_L - r \dot{I}_1 + \dot{U} = 0 \Rightarrow -j\omega L(\dot{I}_1 - \dot{I}) - r \dot{I}_1 + \dot{U} = 0 \Rightarrow \dot{I}_1 = \frac{\dot{U} + j\omega L \dot{I}}{r + j\omega L}$$

$$\text{KVL: } -\dot{E} + (R + 1/j\omega C) \dot{I}_1 - r \dot{I}_1 + \dot{U} = 0 \Rightarrow (R - r + 1/j\omega C) \dot{I}_1 + \dot{U} = \dot{E}$$

$$\Rightarrow (R - r + 1/j\omega C) \frac{\dot{U} + j\omega L \dot{I}}{r + j\omega L} + \dot{U} = \dot{E}$$

$$\Rightarrow \left[\frac{j\omega L \left(R - r + \frac{1}{j\omega C} \right)}{r + j\omega L} \right] \dot{I} + \left[1 + \frac{\left(R - r + \frac{1}{j\omega C} \right)}{r + j\omega L} \right] \dot{U} = \dot{E}$$

$$\dot{E}_T = \dot{U}|_{i=0} = \frac{\dot{E}}{1 + \frac{\left(R - r + \frac{1}{j\omega C} \right)}{r + j\omega L}}$$

$$\dot{J}_N = \dot{I}|_{\dot{U}=0} = \frac{(r + j\omega L) \dot{E}}{j\omega L \left(R - r + \frac{1}{j\omega C} \right)}$$

$$Z_T = \dot{E}_T / \dot{J}_N = \frac{j\omega L \left(R - r + \frac{1}{j\omega C} \right)}{R + j\omega L + \frac{1}{j\omega C}}$$